

# #Assignment 4

## FIELD EFFECT TRANSISTOR

1. Explain the construction and working principle of JFET.
2. Explain the construction and working principle of D-MOSFET and E-MOSFET.
3. Difference between the JFET and bipolar Transistor (BJT).
4. Difference between the JFET and MOSFET.
5. Describe in your own words why  $I_G$  is effectively 0A for a JFET transistor.
6. Sketch the transfer and drain characteristics of an n-channel depletion-type MOSFET with  $I_{DSS} = 12 \text{ mA}$  and  $V_p = -8 \text{ V}$  for a range of  $V_{GS} = -V_p$  to  $V_{GS} = 1 \text{ V}$ .
7. What is the significant difference between the construction of an enhancement-type MOSFET and a depletion-type MOSFET?
8. For the fixed-bias configuration of Fig.1
  - a. Sketch the transfer characteristics of the device.
  - b. Determine the  $I_D$  and  $V_{DS}$ .

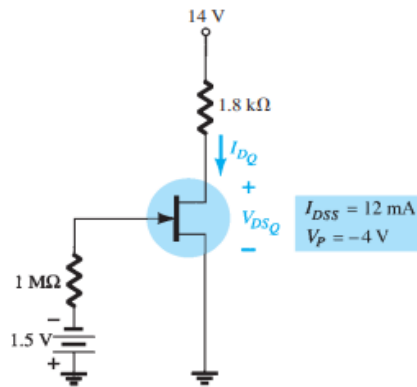


Figure 1

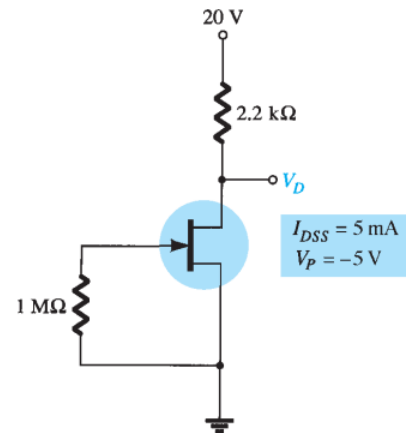


figure 2

9. Determine the  $V_D$  and  $V_{GS}$  for the fixed bias configuration of Fig.2.
10. Given the measurement  $V_s = 1.7 \text{ V}$  for the network of Fig.3
  - a.  $I_D$
  - b.  $V_{GS}$  and  $V_{DS}$ .
  - c.  $I_{DSS}$  and  $V_D$

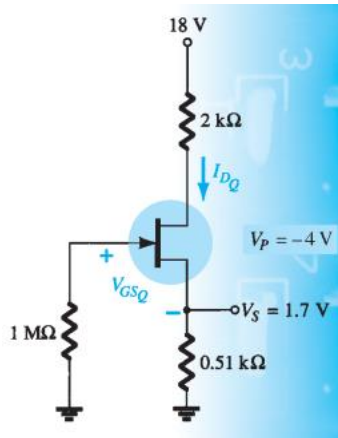


Figure 3

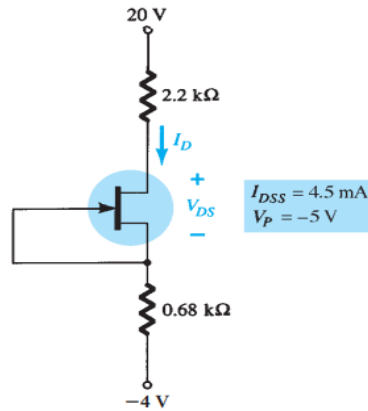


figure 4

11. For the network of Fig.4, determine:

- $I_D$  and  $V_{DS}$
- $V_D$  and  $V_S$

12. Determine the value of  $R_S$  for the network of Fig.5 to establish  $V_D = 10$  V.

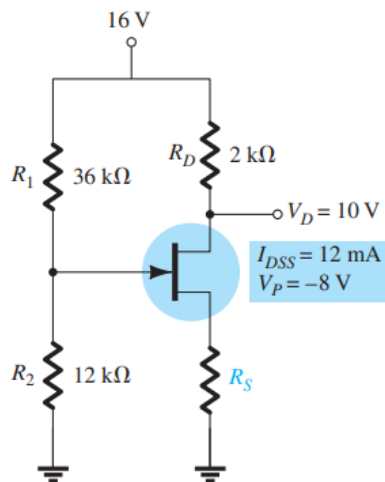


Figure 5

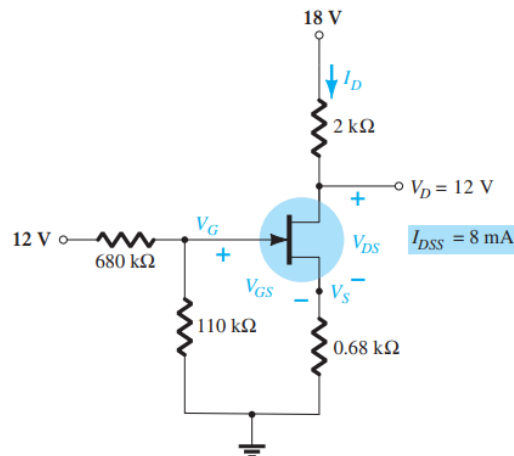


figure 6

13. For the network of Fig.6,  $V_D = 12$  V. Determine:

- $I_D$ ,  $V_S$ ,  $V_{DS}$ ,  $V_G$ ,  $V_{GS}$ , and  $V_P$ .

14. For the network of Fig.7, Determine:

- $I_D$  and  $V_{GS}$
- $V_{DS}$  and  $V_S$ .

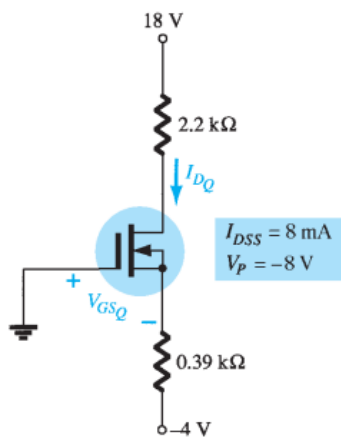


Figure 7

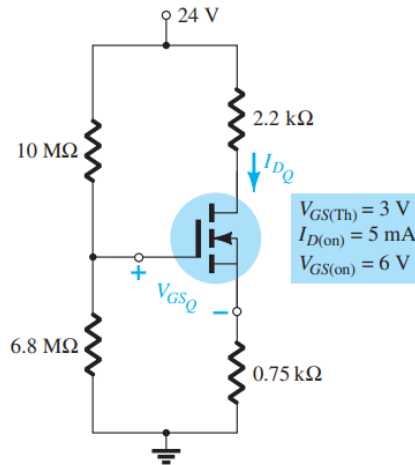


figure 8

15. For the voltage-divider configuration of Fig.8, Determine:
  - a.  $I_D$  and  $V_{GS}$
  - b.  $V_{DS}$  and  $V_S$
16. Determine the  $Z_i$ ,  $Z_o$ , and  $A_v$  for the network of Fig.9 if  $I_{DSS} = 10\text{mA}$ ,  $V_P = -6\text{V}$ , and  $r_d = 40\text{ k}\Omega$ .

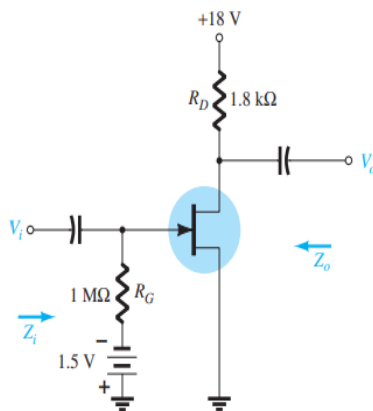


Figure 9

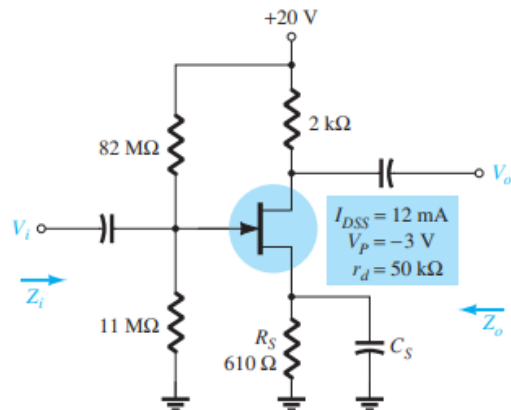


figure 10

17. Determine the  $Z_i$ ,  $Z_o$ , and  $V_o$  for the network of Fig. 10 if  $V_i = 20\text{mV}$ .
18. Derive the expression of transconductance of the JFET.
19. Determine the transconductance  $g_m$  for the MOSFET if  $V_{GS(Th)} = 3\text{V}$  and it is biased at  $V_{GSQ} = 8\text{ V}$ . Assume  $k = 0.3 \times 10^{-3}$ .
20. Determine the value of  $g_m$  for JFET ( $I_{DSS} = 8\text{mA}$ ,  $V_P = -5\text{V}$ ) when biased at  $V_{GSQ} = V_P/4$ .