

#Assignment 3 BJT Small Signal Analysis

1. For the network of Fig.1
 - a. calculates I_B , I_C and r_e .
 - b. Determine Z_i and Z_o .
 - c. calculate voltage gain(A_V).
 - d. Determine the effect of $r_o = 30\text{ K}\Omega$ on A_V .

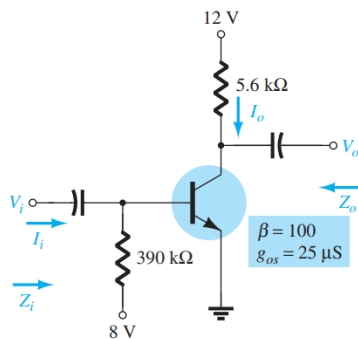


Figure 1

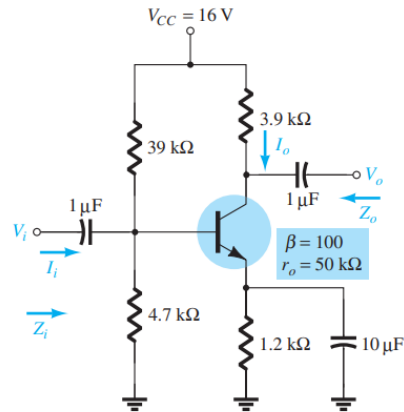


Figure 2

2. For the network of Fig.2
 - a. Determine r_e
 - b. calculates Z_i and Z_o .
 - c. Find A_V
 - d. Repeat parts (b) and (c) with $r_o = 25\text{ K}\Omega$.
3. For the network of Fig.3
 - a. Determine r_e
 - b. Find the dc voltages V_B , V_{CB} and V_{CE} .
 - c. Determine Z_i and Z_o .
 - d. calculate A_V .

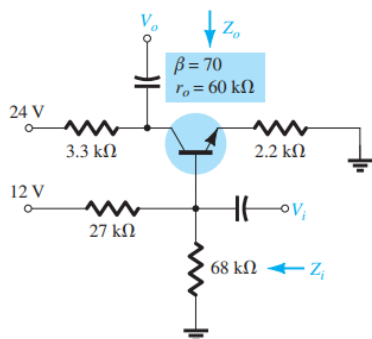


Figure 3

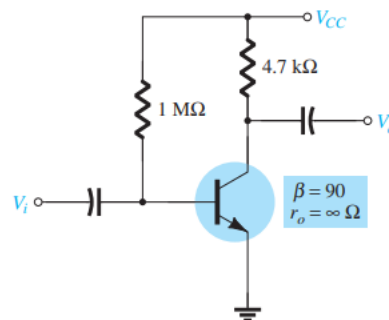


figure 4

4. For the network of Fig 4, determine V_{CC} for a voltage gain of $A_V = -160$.
5. For the network of Fig.5
 - a. Determine r_e
 - b. calculates Z_i and Z_O .
 - c. Find A_V
 - d. Repeat parts (b) and (c) with $r_O = 20 \text{ K}\Omega$.

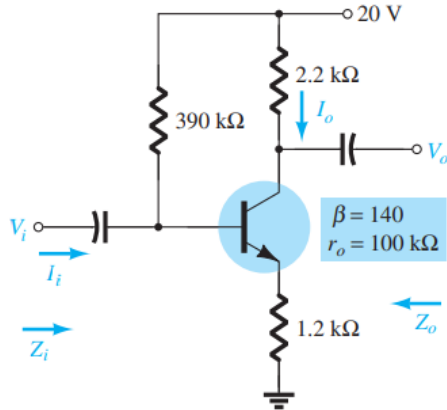


Figure 5

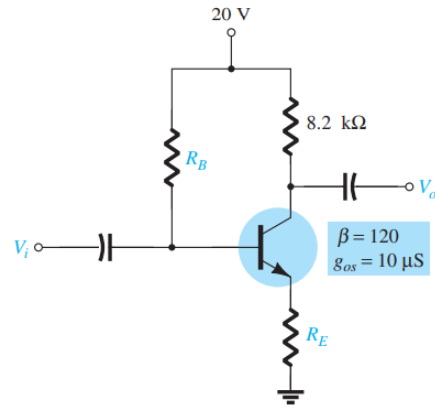


Figure 6

6. For the network of Fig.6, determine R_E and R_B if $A_V = -10$ and $r_e = 3.8 \Omega$. Assume that $Z_b = \beta R_E$.
7. For the network of Fig. 7
 - a. Determine r_e .
 - b. Find Z_i and A_V .

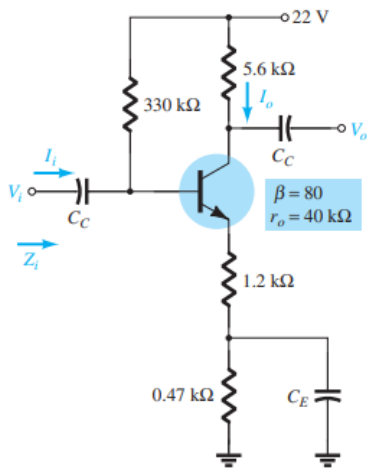


Figure 7

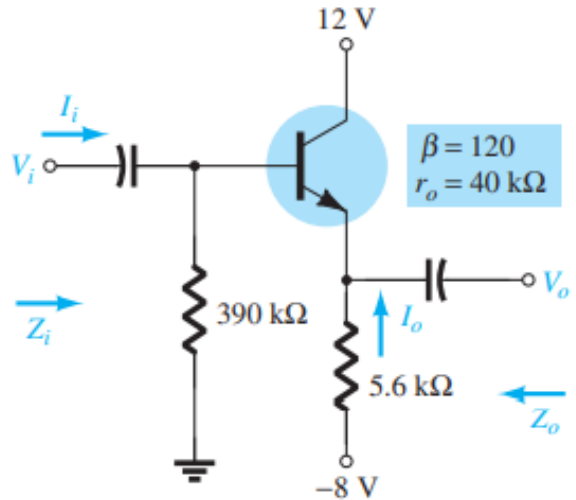


figure 8

8. For the network of Fig.8
- Determine Z_i and Z_o .
 - Find A_v .
 - calculate V_o if $V_i = 1$ mV.
9. For the network of Fig.9, Determine A_v .

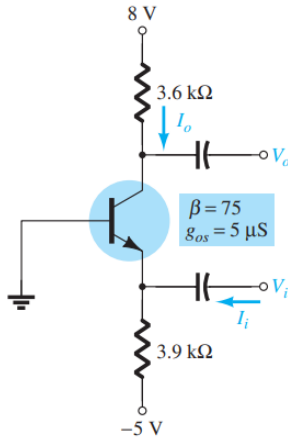


Figure 9

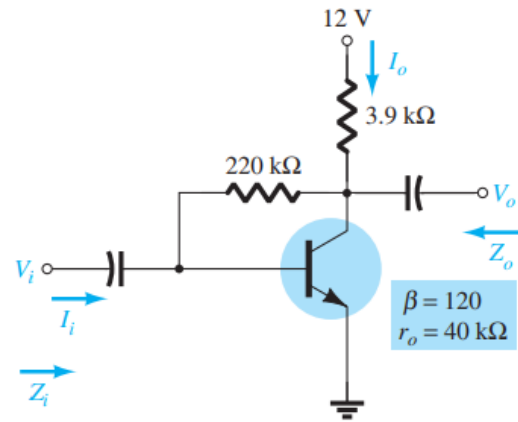


Figure 10

10. For the collector feedback configuration of Fig.10
- Determine r_e .
 - Find Z_i and Z_o .
 - Calculate A_v .
11. Given $r_e = 10\Omega$, $\beta = 200$, $A_v = -160$, and $A_i = 19$ for the network of Fig.11, determine the R_C , R_F , and V_{cc} .

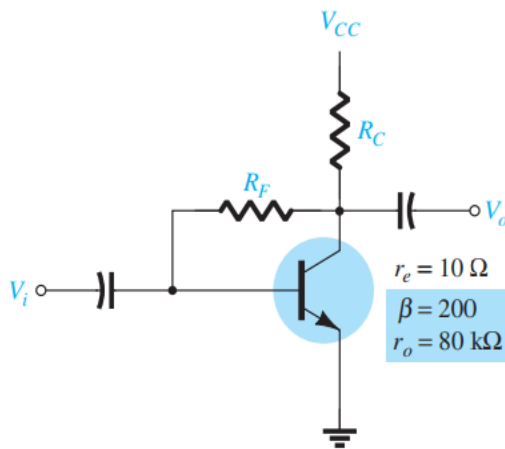


Figure 11

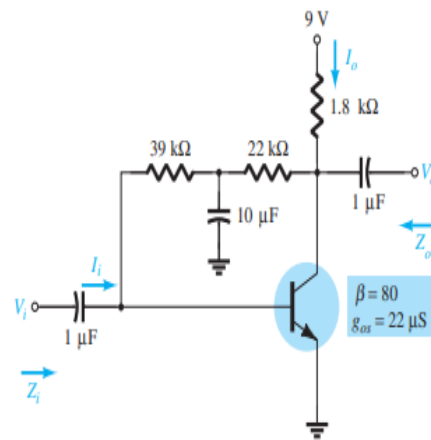


Figure 12

12. For the network of Fig.12
- Determine Z_i and Z_o .
 - Find A_v .